

Circuitos Lógicos e Organização de Computadores

Capítulo 5 – Representação Numérica e Circuitos Aritméticos

Ricardo Pannain

pannain@puc-campinas.edu.br

<http://docentes.puc-campinas.edu.br/ceatec/pannain/>

1

Conversão Decimal-Binária

Convert $(857)_{10}$

		Remainder	
$857 \div 2$	$=$	428	1 LSB
$428 \div 2$	$=$	214	0
$214 \div 2$	$=$	107	0
$107 \div 2$	$=$	53	1
$53 \div 2$	$=$	26	1
$26 \div 2$	$=$	13	0
$13 \div 2$	$=$	6	1
$6 \div 2$	$=$	3	0
$3 \div 2$	$=$	1	1
$1 \div 2$	$=$	0	1 MSB

Result is $(1101011001)_2$

2

Números em diferentes Bases

Decimal	Binary	Octal	Hexadecimal
00	00000	00	00
01	00001	01	01
02	00010	02	02
03	00011	03	03
04	00100	04	04
05	00101	05	05
06	00110	06	06
07	00111	07	07
08	01000	10	08
09	01001	11	09
10	01010	12	0A
11	01011	13	0B
12	01100	14	0C
13	01101	15	0D
14	01110	16	0E
15	01111	17	0F
16	10000	20	10
17	10001	21	11
18	10010	22	12

3

Meio somador (Half-adder)


$$\begin{array}{r}
 x \\
 +y \\
 \hline
 c \ s
 \end{array}
 \qquad
 \begin{array}{r}
 0 \ 0 \\
 +0 \\
 \hline
 0 \ 0
 \end{array}
 \qquad
 \begin{array}{r}
 0 \ 1 \\
 +1 \\
 \hline
 0 \ 1
 \end{array}
 \qquad
 \begin{array}{r}
 1 \ 1 \\
 +0 \\
 \hline
 0 \ 1
 \end{array}
 \qquad
 \begin{array}{r}
 1 \ 1 \\
 +1 \\
 \hline
 1 \ 0
 \end{array}$$

Carry \uparrow \uparrow Sum


(a) The four possible cases

x	y	Carry	Sum
		c	s
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

(b) Truth table

 

(c) Circuit

 

(d) Graphical symbol

4

Adição Binária


$$\begin{array}{r}
 X = x_4x_3x_2x_1x_0 \quad 01111 \quad ?15 ?_{10} \\
 + Y = y_4y_3y_2y_1y_0 \quad 01010 \quad ?10 ?_{10} \\
 \hline
 \quad 1110 \quad \leftarrow \text{Generated carries} \\
 \hline
 S = s_4s_3s_2s_1s_0 \quad 11001 \quad ?25 ?_{10}
 \end{array}$$

5


Somador Completo (Full-adder)

c_i	x_i	y_i	c_{i+1}	s_i
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth table

 


$$s_i = x_i \oplus y_i \oplus c_i$$

 

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$


(b) Karnaugh maps

 

 
(c) Circuit

6

Implementação de um Somador Completo usando decomposição




(a) Block diagram

 

(b) Detailed diagram


7

Somador de n -bits tipo ripple-carry

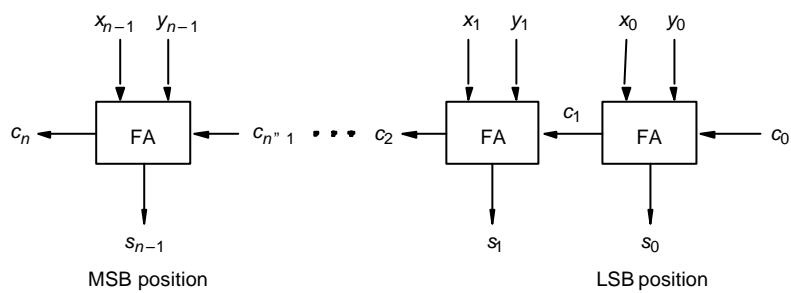


8

 Formatos para representação de números inteiros



(a) Unsigned number

 

(b) Signed number

9

Números inteiros sinalizados com 4 bits

$b_3 b_2 b_1 b_0$	Sign and magnitude	1's complement	2's complement
0111	+7	+7	+7
0110	+6	+6	+6
0101	+5	+5	+5
0100	+4	+4	+4
0011	+3	+3	+3
0010	+2	+2	+2
0001	+1	+1	+1
0000	+0	+0	+0
1000	0	7	8
1001	1	6	7
1010	2	5	6
1011	3	4	5
1100	4	3	4
1101	5	2	3
1110	6	1	2
1111	7	0	1

10

Exemplos de adição em complemento de 1

$$\begin{array}{r}
 (+5) \quad 0101 \\
 +(+2) \quad +0010 \\
 \hline
 (+7) \quad 0111
 \end{array}
 \qquad
 \begin{array}{r}
 ?-5? \quad 1010 \\
 +(+2) \quad +0010 \\
 \hline
 ?-3? \quad 1100
 \end{array}$$

$$\begin{array}{r}
 (+5) \quad 0101 \\
 +?-2? \quad +1101 \\
 \hline
 (+3) \quad 10010 \\
 \leftarrow 1 \\
 \hline
 0011
 \end{array}
 \qquad
 \begin{array}{r}
 ?-5? \quad 1010 \\
 +?-2? \quad +1101 \\
 \hline
 ?-7? \quad 10111 \\
 \leftarrow 1 \\
 \hline
 1000
 \end{array}$$

11

Exemplos de adição em complemento de 2

$$\begin{array}{r}
 (+5) \quad 0101 \\
 +(+2) \quad +0010 \\
 \hline
 (+7) \quad 0111
 \end{array}
 \qquad
 \begin{array}{r}
 ?-5? \quad 1011 \\
 +(+2) \quad +0010 \\
 \hline
 ?-3? \quad 1101
 \end{array}$$

$$\begin{array}{r}
 (+5) \quad 0101 \\
 +?-2? \quad +1110 \\
 \hline
 (+3) \quad 10011 \\
 \uparrow \\
 \text{ignore}
 \end{array}
 \qquad
 \begin{array}{r}
 ?-5? \quad 1011 \\
 +?-2? \quad +1110 \\
 \hline
 ?-7? \quad 11001 \\
 \uparrow \\
 \text{ignore}
 \end{array}$$

12

Exemplos de subtração em complemento de 1

$$\begin{array}{r}
 (+5) \quad 0101 \\
 - (+2) \quad \underline{-0010} \\
 \hline
 (+3) \quad 10011
 \end{array}
 \Rightarrow
 \begin{array}{r}
 0101 \\
 + 1110 \\
 \hline
 10011
 \end{array}$$

↑ ignore

$$\begin{array}{r}
 ?-5? \quad 1011 \\
 - (+2) \quad \underline{-0010} \\
 \hline
 ?-7? \quad 11001
 \end{array}
 \Rightarrow
 \begin{array}{r}
 1011 \\
 + 1110 \\
 \hline
 11001
 \end{array}$$


↑ ignore

$$\begin{array}{r}
 (+5) \quad 0101 \\
 - ?-2? \quad \underline{-1110} \\
 \hline
 (+7) \quad 0111
 \end{array}
 \Rightarrow
 \begin{array}{r}
 0101 \\
 + 0010 \\
 \hline
 0111
 \end{array}$$

$$\begin{array}{r}
 ?-5? \quad 1011 \\
 - ?-2? \quad \underline{-1110} \\
 \hline
 ?-3? \quad 1101
 \end{array}
 \Rightarrow
 \begin{array}{r}
 1011 \\
 + 0010 \\
 \hline
 1101
 \end{array}$$


13

 Interpretação Gráfica de números de 4 bits em complemento de 2



14

Somador / Subtrator

 


15

Exemplo de ocorrência de overflow

$(+7)$	0 1 1 1	$?-7?$	1 0 0 1
$+ (+2)$	<u>+ 0 0 1 0</u>	$+ (+2)$	<u>+ 0 0 1 0</u>
$(+9)$	1 0 0 1	$?-5?$	1 0 1 1
	$c_4 = 0$		$c_4 = 0$
	$c_3 = 1$		$c_3 = 0$
$(+7)$	0 1 1 1	$?-7?$	1 0 0 1
$+ ?-2?$	<u>+ 1 1 1 0</u>	$+ ?-2?$	<u>+ 1 1 1 0</u>
$(+5)$	1 0 1 0 1	$?-9?$	1 0 1 1 1
	$c_4 = 1$		$c_4 = 1$
	$c_3 = 1$		$c_3 = 0$


16

Somador de n -bits tipo ripple-carry

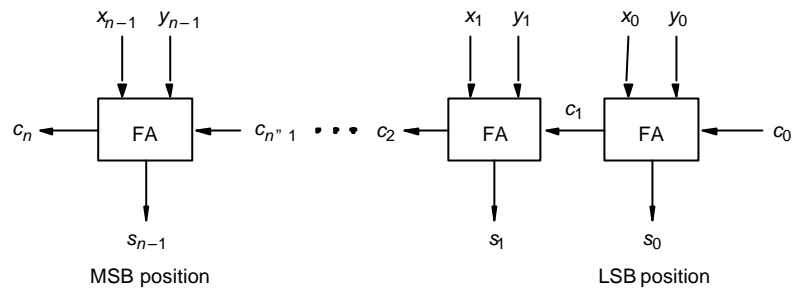

17

 Somador ripple-carry com geração/propagação de sinais




18

Somador carry-lookahead

Como fazer com que um somador trabalhe mais rápido ?


19

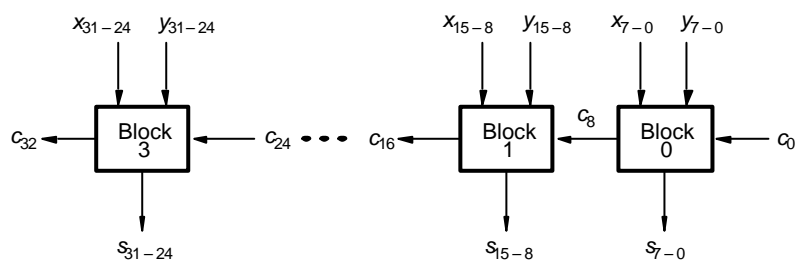Somador carry-lookahead com ripple-carry entre blocos




20

 Dois estágios de um somador carry-lookahead




21

Um somador hierárquico carry-lookahead

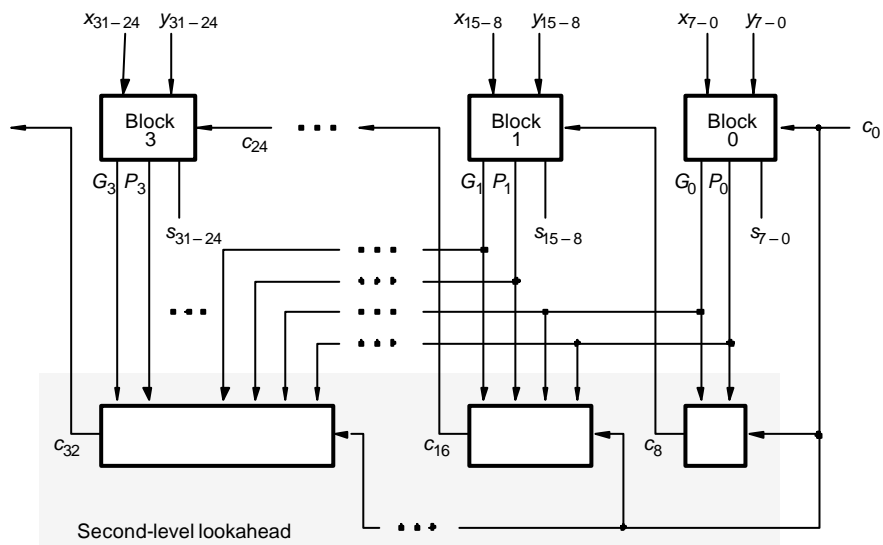


22

 Projeto alternativo para um somador carry-lookahead




23

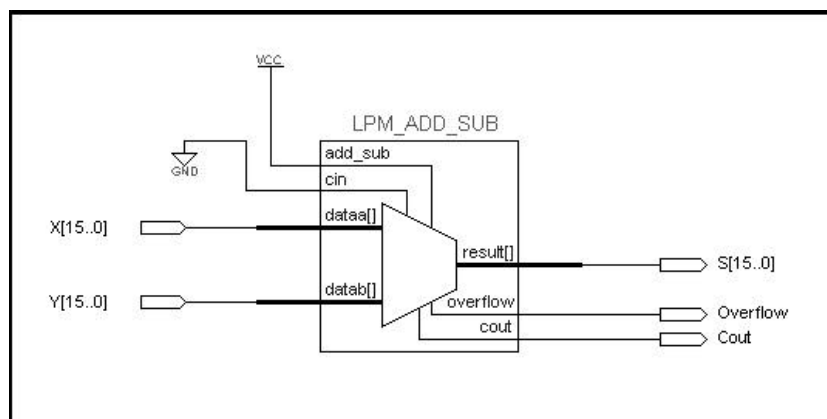Esquemático usando um módulo LPM adder/subtractor




24

 Resultado da simulação de um módulo LPM adder/subtrator



Optimized for cost

 

Optimized for speed

25

Código VHDL para um full-adder

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY fulladd IS
    PORT ( Cin, x, y : IN     STD_LOGIC ;
          s, Cout    : OUT    STD_LOGIC ) ;
END fulladd ;

ARCHITECTURE LogicFunc OF fulladd IS
BEGIN
    s <= x XOR y XOR Cin ;
    Cout <= (x AND y) OR (Cin AND x) OR (Cin AND y) ;
END LogicFunc ;
    
```

26

Código VHDL para um somador de 4 bits

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY adder4 IS
    PORT ( Cin      : IN      STD_LOGIC ;
          x3, x2, x1, x0 : IN      STD_LOGIC ;
          y3, y2, y1, y0 : IN      STD_LOGIC ;
          s3, s2, s1, s0 : OUT     STD_LOGIC ;
          Cout       : OUT     STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL c1, c2, c3 : STD_LOGIC ;
    COMPONENT fulladd
        PORT ( Cin, x, y : IN      STD_LOGIC ;
              s, Cout  : OUT     STD_LOGIC ) ;
    END COMPONENT ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, x0, y0, s0, c1 ) ;
    stage1: fulladd PORT MAP ( c1, x1, y1, s1, c2 ) ;
    stage2: fulladd PORT MAP ( c2, x2, y2, s2, c3 ) ;
    stage3: fulladd PORT MAP (
        Cin => c3, Cout => Cout, x => x3, y => y3, s => s3 ) ;
END Structure ;
```

27

Declaração de um Package

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

PACKAGE fulladd_package IS
    COMPONENT fulladd
        PORT ( Cin, x, y : IN      STD_LOGIC ;
              s, Cout  : OUT     STD_LOGIC ) ;
    END COMPONENT ;
END fulladd_package ;
```

28

Usando um package para somador de 4 bits

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;

ENTITY adder4 IS
    PORT ( Cin      : IN    STD_LOGIC ;
          x3, x2, x1, x0 : IN    STD_LOGIC ;
          y3, y2, y1, y0 : IN    STD_LOGIC ;
          s3, s2, s1, s0 : OUT   STD_LOGIC ;
          Cout      : OUT   STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL c1, c2, c3 : STD_LOGIC ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, x0, y0, s0, c1 ) ;
    stage1: fulladd PORT MAP ( c1, x1, y1, s1, c2 ) ;
    stage2: fulladd PORT MAP ( c2, x2, y2, s2, c3 ) ;
    stage3: fulladd PORT MAP (
        Cin => c3, Cout => Cout, x => x3, y => y3, s
        => s3 ) ;
END Structure ;
```

29

Somador de 4 bits usando sinais multibit

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.fulladd_package.all ;

ENTITY adder4 IS
    PORT ( Cin      : IN    STD_LOGIC ;
          X, Y      : IN    STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          S         : OUT   STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          Cout      : OUT   STD_LOGIC ) ;
END adder4 ;

ARCHITECTURE Structure OF adder4 IS
    SIGNAL C : STD_LOGIC_VECTOR(1 TO 3) ;
BEGIN
    stage0: fulladd PORT MAP ( Cin, X(0), Y(0), S(0), C(1) ) ;
    stage1: fulladd PORT MAP ( C(1), X(1), Y(1), S(1), C(2) ) ;
    stage2: fulladd PORT MAP ( C(2), X(2), Y(2), S(2), C(3) ) ;
    stage3: fulladd PORT MAP ( C(3), X(3), Y(3), S(3), Cout ) ;
END Structure ;
```

30

Código VHDL code para um somador de 16-bit

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;

ENTITY adder16 IS
    PORT ( X, Y : IN     STD_LOGIC_VECTOR(15 DOWNTO 0) ;
          S   : OUT    STD_LOGIC_VECTOR(15 DOWNTO 0) ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
BEGIN
    S <= X + Y ;
END Behavior ;
```

31

Somador de 16-bit com carry e overflow

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;

ENTITY adder16 IS
    PORT ( Cin           : IN     STD_LOGIC ;
          X, Y           : IN     STD_LOGIC_VECTOR(15 DOWNTO 0) ;
          S              : OUT    STD_LOGIC_VECTOR(15 DOWNTO 0) ;
          Cout, Overflow : OUT    STD_LOGIC ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
    SIGNAL Sum : STD_LOGIC_VECTOR(16 DOWNTO 0) ;
BEGIN
    Sum <= ('0' & X) + Y + Cin ;
    S <= Sum(15 DOWNTO 0) ;
    Cout <= Sum(16) ;
    Overflow <= Sum(16) XOR X(15) XOR Y(15) XOR Sum(15) ;
END Behavior ;
```

32

Use of the arithmetic Uso de package com circuito aritmético

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_arith.all ;

ENTITY adder16 IS
    PORT ( Cin           : IN    STD_LOGIC ;
          X, Y           : IN    SIGNED(15 DOWNTO 0) ;
          S              : OUT   SIGNED(15 DOWNTO 0) ;
          Cout, Overflow : OUT   STD_LOGIC ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
    SIGNAL Sum : SIGNED(16 DOWNTO 0) ;
BEGIN
    Sum <= ('0' & X) + Y + Cin ;
    S <= Sum(15 DOWNTO 0) ;
    Cout <= Sum(16) ;
    Overflow <= Sum(16) XOR X(15) XOR Y(15) XOR Sum(15) ;
END Behavior ;
```

33

Um somador de 16-bit adder usando sinais INTEGER

```
ENTITY adder16 IS
    PORT ( X, Y : IN    INTEGER RANGE -32768 TO 32767 ;
          S    : OUT   INTEGER RANGE -32768 TO 32767 ) ;
END adder16 ;

ARCHITECTURE Behavior OF adder16 IS
BEGIN
    S <= X + Y ;
END Behavior ;
```

34

Circuito multiplicador 4 X 4

$$\begin{array}{r}
 \text{Multiplicand M (14)} \quad 1110 \\
 \text{Multiplier Q (11)} \quad \underline{?1011} \\
 \phantom{\text{Multiplier Q (11)}} \quad 1110 \\
 \phantom{\text{Multiplier Q (11)}} \quad 1110 \\
 \phantom{\text{Multiplier Q (11)}} \quad 0000 \\
 \phantom{\text{Multiplier Q (11)}} \quad \underline{1110} \\
 \text{Product P (154)} \quad 10011010
 \end{array}$$

(a) Multiplication by hand

35


Circuito multiplicador 4 X 4

$$\begin{array}{r}
 \text{Multiplicand M (11)} \quad 1110 \\
 \text{Multiplier Q (14)} \quad \underline{?1011} \\
 \text{Partial product 0} \quad 1110 \\
 \phantom{\text{Partial product 0}} \quad + 1110 \quad | \\
 \text{Partial product 1} \quad 10101 \\
 \phantom{\text{Partial product 1}} \quad + 0000 \quad | \\
 \text{Partial product 2} \quad 01010 \\
 \phantom{\text{Partial product 2}} \quad + 1110 \quad | \downarrow \\
 \text{Product P (154)} \quad 10011010
 \end{array}$$


(b) Implementação da multiplicação em hardware

36

Circuito multiplicador 4 X 4

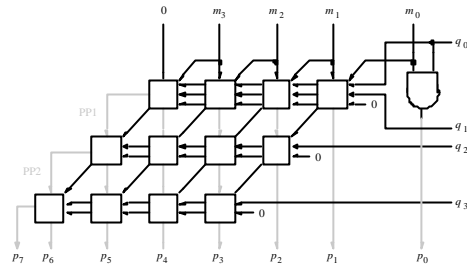

(a) Structure of the circuit

 

(b) A block in the top row

(c) A block in the bottom two rows

37

Multiplicação de números sinalizados

Multiplicand M	(+14)	0 1 1 1 0
Multiplier Q	(+11)	x 0 1 0 1 1
Partial product 0		0 0 0 1 1 1 0
		+ 0 0 1 1 1 0
Partial product 1		0 0 1 0 1 0 1
		+ 0 0 0 0 0 0
Partial product 2		0 0 0 1 0 1 0
		+ 0 0 1 1 1 0
Partial product 3		0 0 1 0 0 1 1
		+ 0 0 0 0 0 0
Product P	(+154)	0 0 1 0 0 1 1 0 1 0

(a) Positive multiplicand

38


Multiplicação de números sinalizados

Multiplicand M	(-14)	1 0 0 1 0
Multiplier Q	(+11)	? ? 0 1 0 1 1
Partial product 0		1 1 1 0 0 1 0
		+ 1 1 0 0 1 0
Partial product 1		1 1 0 1 0 1 1
		+ 0 0 0 0 0 0
Partial product 2		1 1 1 0 1 0 1
		+ 1 1 0 0 1 0
Partial product 3		1 1 0 1 1 0 0
		+ 0 0 0 0 0 0
Product P	(-154)	1 1 0 1 1 0 0 1 1 0

 
(b) Negative multiplicand

39

Padrão IEEE 754 standard número de ponto flutuante



(a) Single precision

 

(c) Double precision

40

Código BCD – Binary Code Decimal

Decimal digit	BCD code
0	0000
1	0001
2	0010
3	0011
4	0100
5	0101
6	0110
7	0111
8	1000
9	1001

41


Adição em BCD

$$\begin{array}{r}
 X \quad 0111 \quad 7 \\
 + Y \quad +0101 \quad +5 \\
 \hline
 Z \quad 1100 \quad 12 \\
 \quad +0110 \\
 \hline
 \text{carry} \rightarrow \underbrace{10010}_{S=2}
 \end{array}$$

$$\begin{array}{r}
 X \quad 1000 \quad 8 \\
 + Y \quad +1001 \quad +9 \\
 \hline
 Z \quad 10001 \quad 17 \\
 \quad +0110 \\
 \hline
 \text{carry} \rightarrow \underbrace{10111}_{S=7}
 \end{array}$$

42

 Somador BCD de um dígito – diagrama de blocos



43

Somador BCD de um dígito – código VHDL

```

LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;


ENTITY BCD IS
    PORT ( X, Y      : IN   STD_LOGIC_VECTOR(3 DOWNTO 0) ;
          S         : OUT  STD_LOGIC_VECTOR(4 DOWNTO 0) ) ;
END BCD ;

ARCHITECTURE Behavior OF BCD IS
    SIGNAL Z : STD_LOGIC_VECTOR(4 DOWNTO 0) ;
    SIGNAL Adjust : STD_LOGIC ;
BEGIN
    Z <= ('0' & X) + Y ;
    Adjust <= '1' WHEN Z > 9 ELSE '0' ;
    S <= Z WHEN (Adjust = '0') ELSE Z + 6 ;
END Behavior ;


```

44

Simulação de um somador BCD de um dígito

 

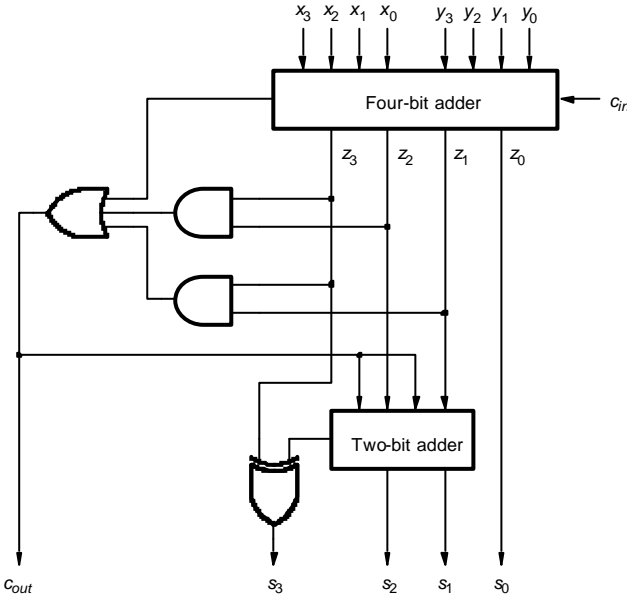Circuito para um somador BCD de um dígito



Bit positions	Bit positions 054							
3210	000	001	010	011	100	101	110	111
0000	NUL	DLE	SPACE	0	@	P	'	p
0001	SOH	DC1	!	1	A	Q	a	q
0010	STX	DC2	"	2	B	R	b	r
0011	ETX	DC3	#	3	C	S	c	s
0100	EOT	DC4	\$	4	D	T	d	t
0101	ENQ	NAK	%	5	E	U	e	u
0110	ACK	SYN	&	6	F	V	f	v
0111	BEL	ETB	'	7	G	W	g	w
1000	BS	CAN	(8	H	X	h	x
1001	HT	EM)	9	I	Y	i	y
1010	LF	SUB	*	:	J	Z	j	z
1011	VT	ESC	+	;	K	[k	{
1100	FF	FS	,	<	L	\	l	
1101	CR	GS	=	=	M]	m	}
1110	SO	RS	.	>	N	^	n	~
1111	SI	US	/	?	O	o	o	DEL
NUL	Null/ldle		SI	Shift in				
SOH	Start of header		DLE	Data link escape				
STX	Start of text		DC1 DC4	Device control				
ETX	End of text		NAK	Negative acknowledgment				
EOT	End of transmitted		SYN	Synchronous idle				
ENQ	Enquiry		ETB	End of transmitted block				
ACK	Acknowledgement		CAN	Cancel (error in data)				
BEL	Audible signal		EM	End of medium				
BS	Back space		SUB	Special sequence				
HT	Horizontal tab		ESC	Escape				
LF	Line feed		FS	File separator				
VT	Vertical tab		GS	Group separator				
FF	Form feed		RS	Record separator				
CR	Carriage return		US	Unit separator				
SO	Shift out		DEL	Delete/ldle				

Bit positions of code format = 6 5 4 3 2 1 0