

# Circuitos Lógicos e Organização de Computadores

## Capítulo 7 – Flip-Flops e Circuitos Seqüenciais

Ricardo Pannain

[pannain@puc-campinas.edu.br](mailto:pannain@puc-campinas.edu.br)


<http://docentes.puc-campinas.edu.br/ceatec/pannain/>

# Circuito Seqüenciais


Circuito combinacional ✎ saídas dependem apenas das entradas

Circuito seqüencial ✎ saídas dependem das entradas e do comportamento anterior do circuito


Exemplo - Controle de Sistema de Alarme

 


### Elemento de memória simples

 


### Elemento de memória com portas NOR

 

### Elemento de memória controlado

 


# Latch construído com portas NOR

 

(a) Circuito


| S | R | $Q_a$ | $Q_b$           |
|---|---|-------|-----------------|
| 0 | 0 | 0/1/0 | (sem alteração) |
| 0 | 1 | 0     | 1               |
| 1 | 0 | 1     | 0               |
| 1 | 1 | 0     | 0               |

(b) Tabela Verdade

 

(c) Diagrama de Tempo


## Latch SR com clock (gated)

 


(a) Circuito

| Clk | S | R | $Q(t+1)$               |
|-----|---|---|------------------------|
| 0   | x | x | $Q(t)$ (sem alteração) |
| 1   | 0 | 0 | $Q(t)$ (sem alteração) |
| 1   | 0 | 1 | 0                      |
| 1   | 1 | 0 | 1                      |
| 1   | 1 | 1 | x                      |

(b) Tabela Verdade

 


(c) Timing diagram

 


(d) Símbolo Gráfico

## Latch SR Gated SR com portas NAND

 


## Latch D Gated

 


(a) Circuito

| Clk | D | Q?? + 1?? |
|-----|---|-----------|
| 0   | x | Q???      |
| 1   | 0 | 0         |
| 1   | 1 | 1         |

(b) Tabela Verdade

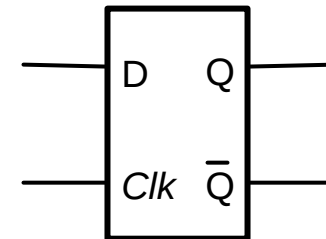


(c) Símbolo Gráfico

 

(d) Diagrama de Tempo

## Setup and hold times

 


Setup time ✎ tempo mínimo que D deve estar estável antes da descida do clock


Hold time ✎ temp mínimo que D deve ser mantido estável após a descida do clock

Valores típos (CMOS):  $t_{su} = 3\text{ns}$  e  $t_h = 2\text{ns}$


## Flip-Flop D Master-slave

 

(a) Circuito

 

(c) Símbolo Gráfico

 


(b) Diagrama de tempo

CLK = 1 master armazena  
e slave não muda


CLK = 0 master não muda  
e slave armazena

Sensível à borda de descida
 
## Flip-Flop D sensível à borda de subida



(a) Circuito

 

(b) Símbolo Gráfico

Clk = 0  $\Rightarrow$  P1 = P2 = 1

P3 = D


P4 = D

Clk = 1  $\Rightarrow$  P3 e P4 são transmitidos através de 2 e 3


$\Rightarrow$  P1 =  $\overline{D}$  e P2 = D  $\Rightarrow$  Q = D e  $\overline{Q} = \overline{D}$

Obs - P4 e P3 DEVEM ESTAR ESTÁVEIS QUANDO CLK MUDA PARA 1
 
## Comparação de Flip-Flops D sensíveis a nível e sensíveis a borda




(a) Circuito

 


(b) Diagrama de Tempo
 
## Flip-Flop Master-slave tipo D com *Clear* e *Preset*




(a) Circuito

 


(b) Símbolo Gráfico
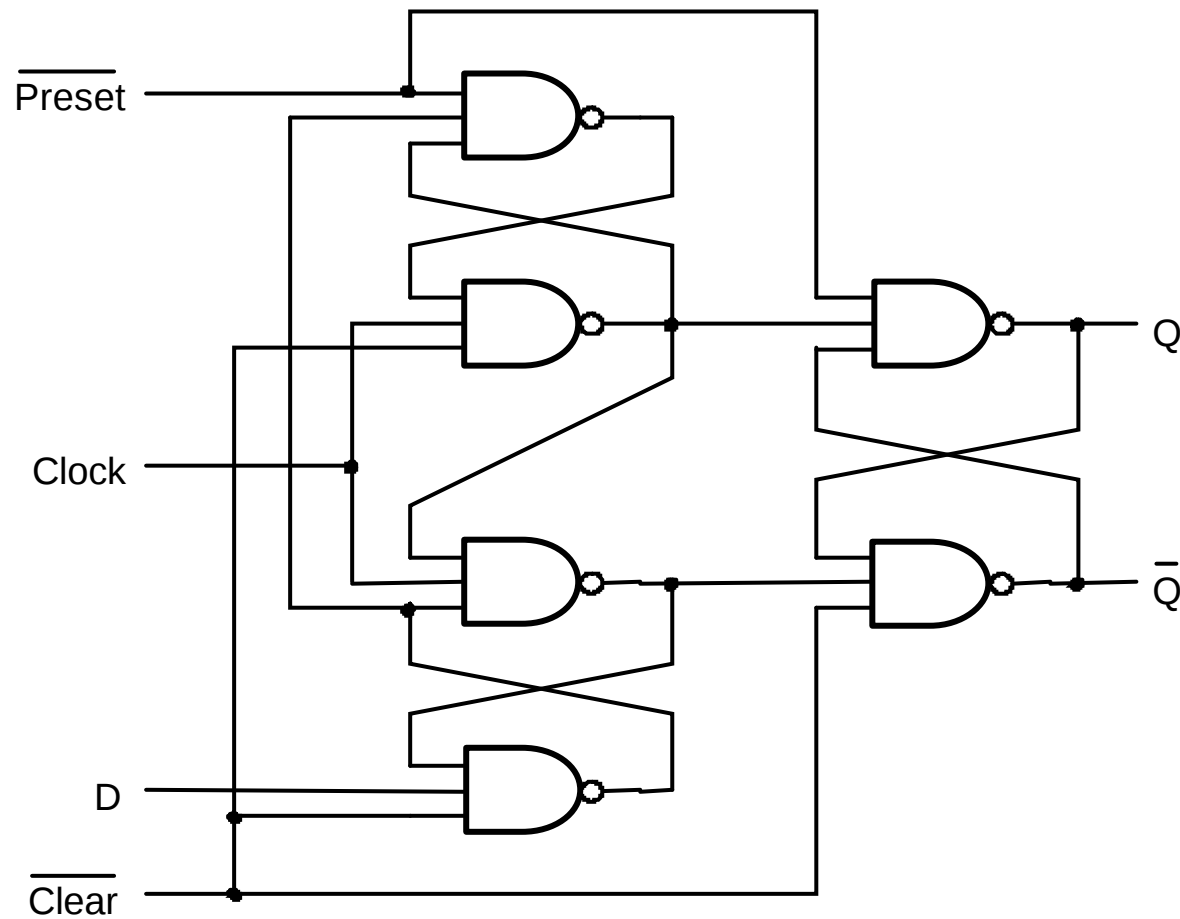
## Flip-Flop D sensível à borda de subida com *Clear* e *Preset*




(a) Circuito

 


(b) Símbolo Gráfico

## Flip-Flop D com reset síncrono

 


## Flip-Flop tipo T (toogle)

 


(a) Circuito

| T | $Q_{n+1}$   |
|---|-------------|
| 0 | $Q_n$       |
| 1 | $\bar{Q}_n$ |

(b) Tabela Verdade

 


(c) Símbolo Gráfico

 

(d) Diagrama de tempo

## Flip-Flop JK

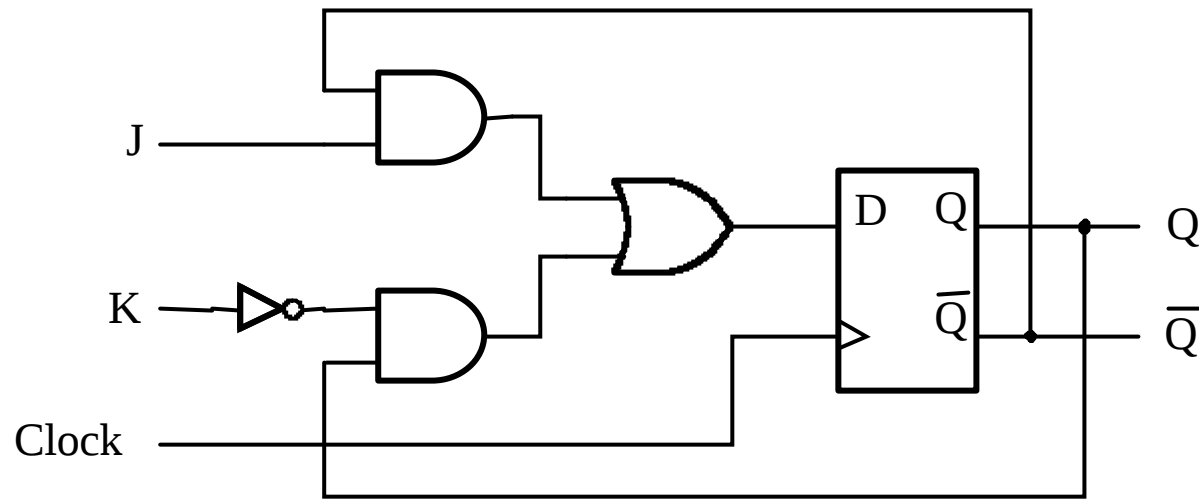

$$D = J \bar{Q} + \bar{K} Q$$


J e K ~~de~~ entradas  
De controle

FFs SR e T juntos

(a) Circuito

| J | K | $Q_{t+1}$   |
|---|---|-------------|
| 0 | 0 | $Q_t$       |
| 0 | 1 | 0           |
| 1 | 0 | 1           |
| 1 | 1 | $\bar{Q}_t$ |


(b) Tabela Verdade

 

(c) Símbolo Gráfico
 
# Registrador de deslocamento com entrada e saída serial

Registrador é um conjunto de n Flip-Flops



(a) Circuito


|                | In | Q <sub>1</sub> | Q <sub>2</sub> | Q <sub>3</sub> | Q <sub>4</sub> = Out |
|----------------|----|----------------|----------------|----------------|----------------------|
| t <sub>0</sub> | 1  | 0              | 0              | 0              | 0                    |
| t <sub>1</sub> | 0  | 1              | 0              | 0              | 0                    |
| t <sub>2</sub> | 1  | 0              | 1              | 0              | 0                    |
| t <sub>3</sub> | 1  | 1              | 0              | 1              | 0                    |
| t <sub>4</sub> | 1  | 1              | 1              | 0              | 1                    |
| t <sub>5</sub> | 0  | 1              | 1              | 1              | 0                    |
| t <sub>6</sub> | 0  | 0              | 1              | 1              | 1                    |
| t <sub>7</sub> | 0  | 0              | 0              | 1              | 1                    |

FFs master-slave  
ou sensível à borda.

***Porque não  
sensível a nível ?***


(b) Exemplo de uma sequência
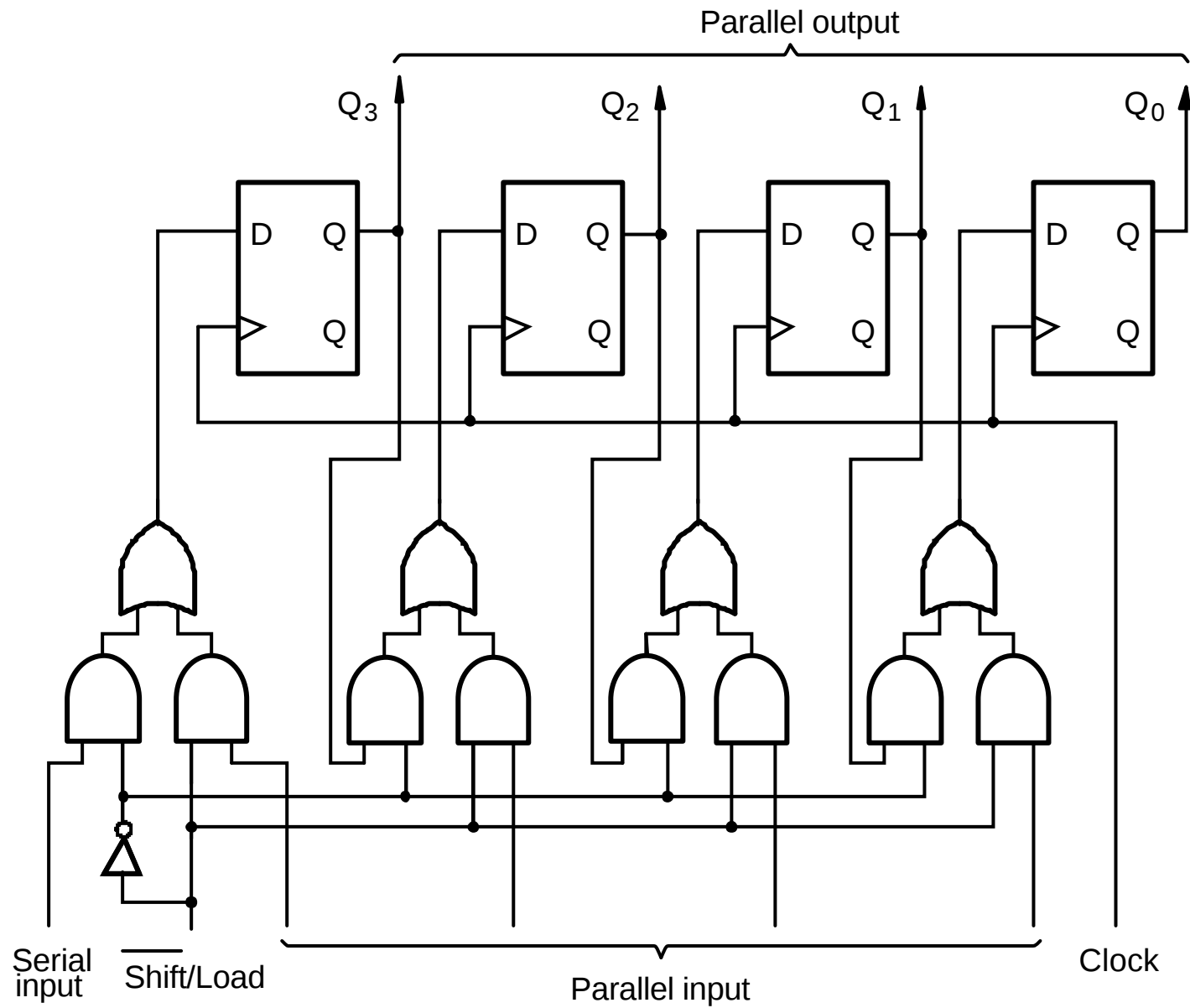
## Registrador de deslocamento com entrada paralela e serial e saída paralela




# Contadores

## Contador de 3 bits up-counter

 


(a) Circuito

 


(b) Diagrama de tempo

## Contador de 3 bits down-counter

 


(a) Circuit

 


(b) Timing diagram

 
## Derivação de contador síncrono up-counter


 
## Contador síncrono de quatro-bits up-counter




(a) Circuito

 


(b) Diagrama de tempo


## Inclusão de sinais de enable e clear

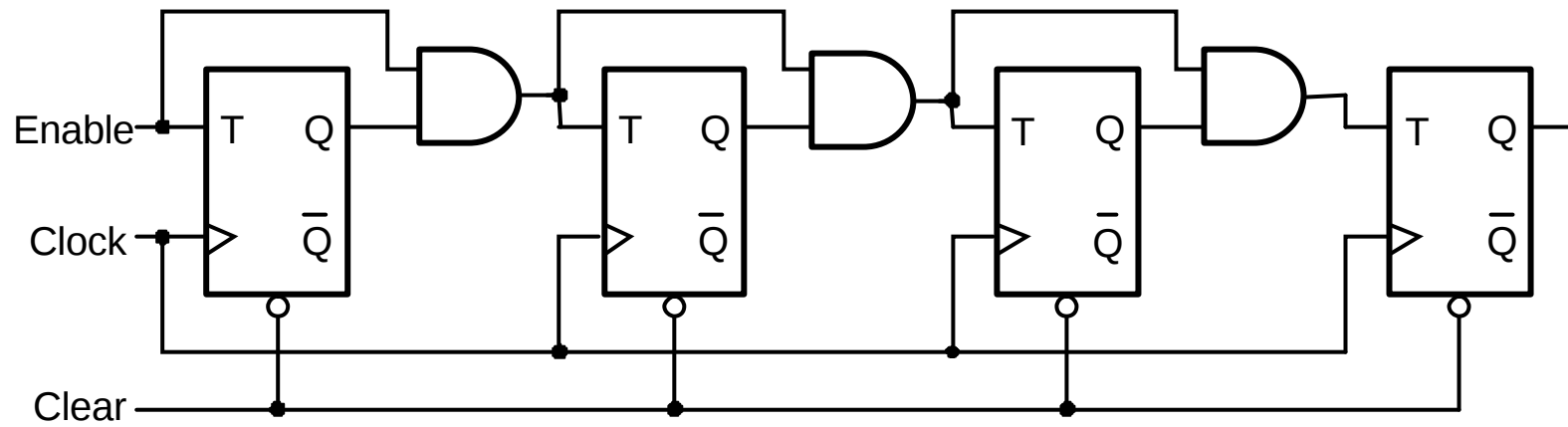


Contador de 4 bits com FF D

 


Contador com entrada paralela

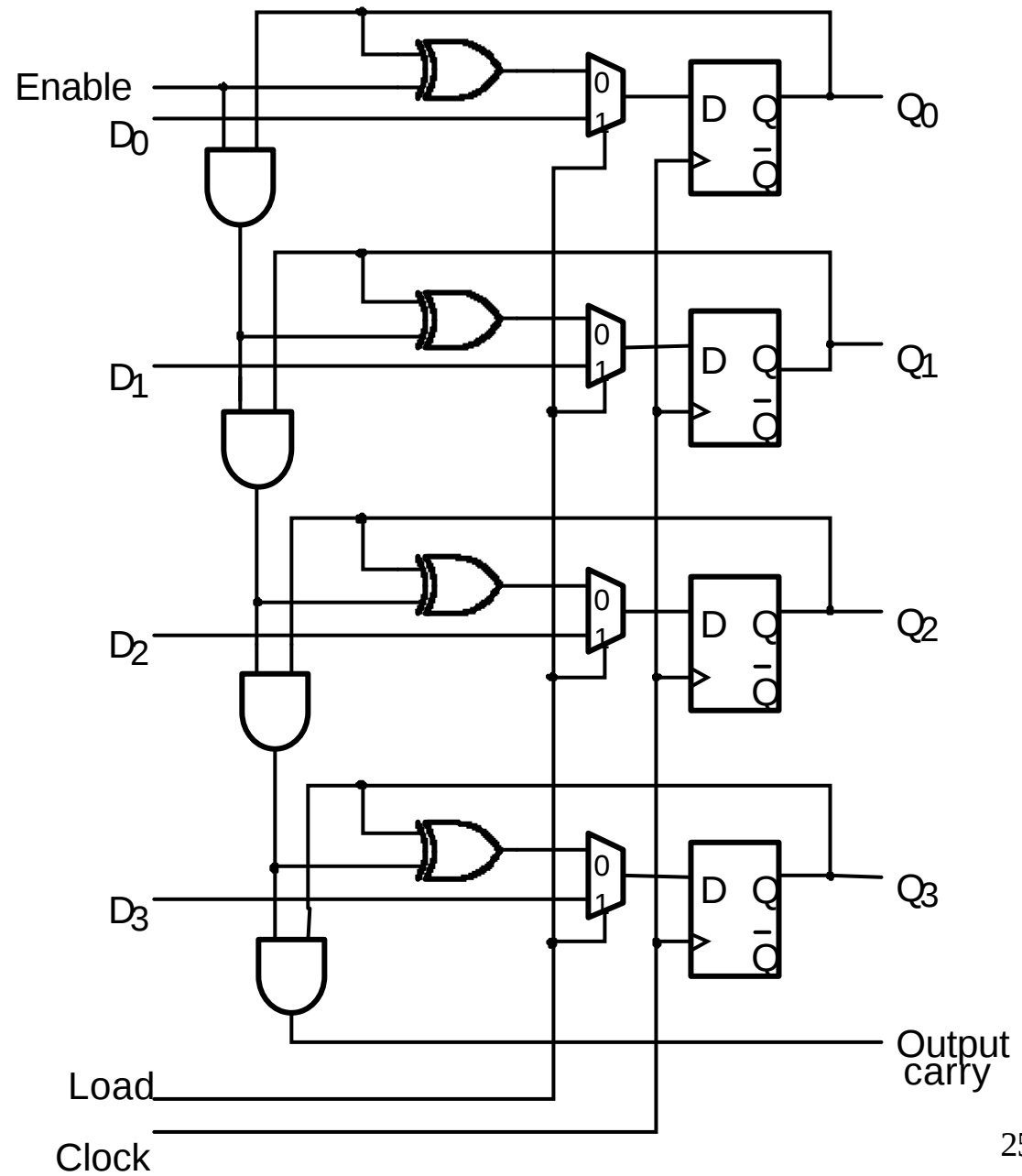

## Contador modulo-6 com reset síncrono

 


(a) Circuito

 


(b) Diagrama de tempo

## Contador modulo-6 com reset síncrono

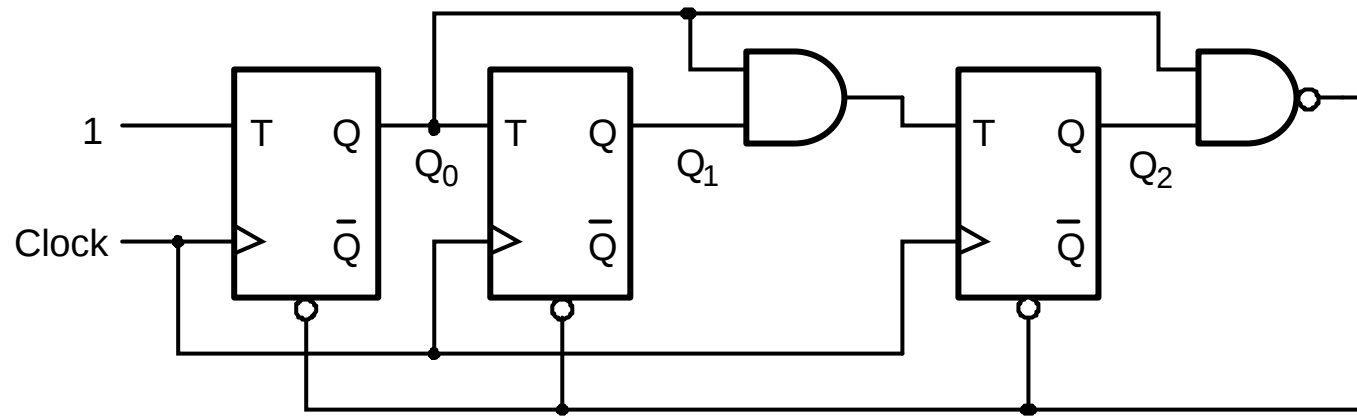



(a) Circuito

 

(b) Diagrama de tempo

## Contador BCD de 2 dígitos

 


 

(a) An  $n$ -bit ring counter


Contador em Anel

1000, 0100, 0010, 0001

 

(b) A four-bit ring counter

## Contador Johnson

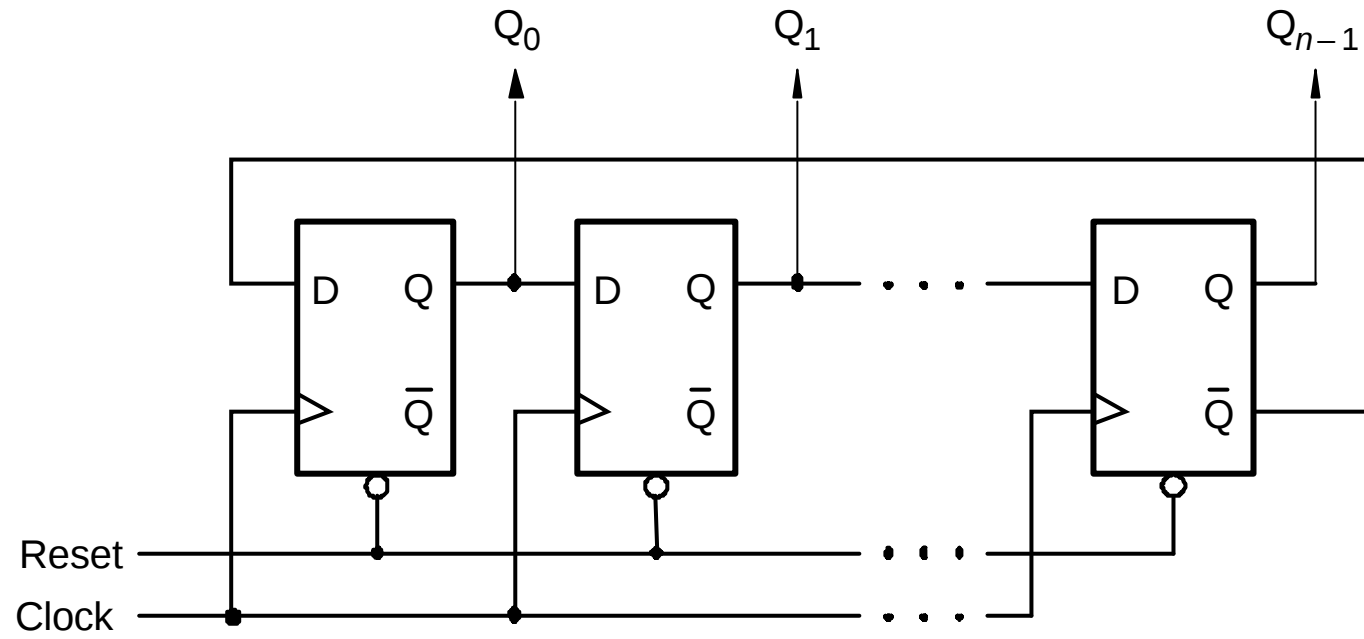

## Inatalação de um FF D de um package

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
LIBRARY altera ;
USE altera.maxplus2.all ;

ENTITY flipflop IS
    PORT ( D, Clock          : IN      STD_LOGIC ;
           Resetn, Presetn   : IN      STD_LOGIC ;
           Q                  : OUT     STD_LOGIC ) ;
END flipflop ;

ARCHITECTURE Structure OF flipflop IS
BEGIN
    dff_instance: dff PORT MAP ( D, Clock, Resetn, Presetn, Q ) ;
END Structure ;
```

## Memória

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY implied IS
    PORT (  A, B      : IN      STD_LOGIC ;
           AeqB      : OUT     STD_LOGIC ) ;
END implied ;

ARCHITECTURE Behavior OF implied IS
BEGIN
    PROCESS ( A, B )
    BEGIN
        IF A = B THEN
            AeqB <= '1' ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

## Codigo para um latch D gated

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY latch IS
    PORT ( D, Clk : IN      STD_LOGIC ;
          Q       : OUT     STD_LOGIC) ;
END latch ;

ARCHITECTURE Behavior OF latch IS
BEGIN
    PROCESS ( D, Clk )
    BEGIN
        IF Clk = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

## Código para um FF D

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Clock : IN    STD_LOGIC ;
           Q         : OUT  STD_LOGIC) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        IF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

## Código para um FF D usando WAIT UNTIL

```
LIBRARY ieee;
USE ieee.std_logic_1164.all;

ENTITY flipflop IS
    PORT ( D, Clock : IN      STD_LOGIC ;
          Q          : OUT    STD_LOGIC ) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        Q <= D ;
    END PROCESS ;
END Behavior ;
```

## FF D com reset assíncrono

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Resetn, Clock : IN      STD_LOGIC ;
          Q                  : OUT    STD_LOGIC);
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

## FF D com reset síncrono

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY flipflop IS
    PORT ( D, Resetn, Clock : IN      STD_LOGIC ;
          Q                 : OUT    STD_LOGIC) ;
END flipflop ;

ARCHITECTURE Behavior OF flipflop IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF Resetn = '0' THEN
            Q <= '0' ;
        ELSE
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

## Instanciação do módulo *lpm\_shiftreg*

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
LIBRARY lpm ;
USE lpm.lpm_components.all ;

ENTITY shift IS
    PORT ( Clock      : IN      STD_LOGIC ;
           Reset       : IN      STD_LOGIC ;
           Shiftin, Load : IN      STD_LOGIC ;
           R           : IN      STD_LOGIC_VECTOR(3 DOWNT0 0) ;
           Q           : OUT     STD_LOGIC_VECTOR(3 DOWNT0 0) ) ;
END shift ;

ARCHITECTURE Structure OF shift IS
BEGIN
    instance: lpm_shiftreg
        GENERIC MAP (LPM_WIDTH => 4, LPM_DIRECTION => "RIGHT")
        PORT MAP (data => R, clock => Clock, aclr => Reset,
                  load => Load, shiftin => Shiftin, q => Q ) ;
END Structure ;
```

## Código um registrador de 8 bits com clear assíncrono

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY reg8 IS
    PORT ( D          : IN    STD_LOGIC_VECTOR(7 DOWNTO 0) ;
          Resetn, Clock : IN    STD_LOGIC ;
          Q            : OUT   STD_LOGIC_VECTOR(7 DOWNTO 0) ) ;
END reg8 ;

ARCHITECTURE Behavior OF reg8 IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= "00000000" ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

## Código um registrador de $n$ -bit com clear assíncrono

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY regn IS
    GENERIC ( N : INTEGER := 16 ) ;
    PORT ( D          : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
           Resetn, Clock : IN      STD_LOGIC ;
           Q           : OUT     STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END regn ;

ARCHITECTURE Behavior OF regn IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= (OTHERS => '0') ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Q <= D ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

Código para um FF D com um multiplexador 2-para-1 na entrada *D*

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY muxdff IS
    PORT ( D0, D1, Sel, Clock : IN      STD_LOGIC ;
           Q                  : OUT    STD_LOGIC ) ;
END muxdff ;

ARCHITECTURE Behavior OF muxdff IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF Sel = '0' THEN
            Q <= D0 ;
        ELSE
            Q <= D1 ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

## Código hierárquico para um shift-register de 4 bits

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY shift4 IS
    PORT ( R          : IN          STD_LOGIC_VECTOR(3 DOWNT0 0) ;
           L, w, Clock : IN          STD_LOGIC ;
           Q          : BUFFER      STD_LOGIC_VECTOR(3 DOWNT0 0) ) ;
END shift4 ;

ARCHITECTURE Structure OF shift4 IS
    COMPONENT muxdff
        PORT ( D0, D1, Sel, Clock : IN          STD_LOGIC ;
              Q                  : OUT          STD_LOGIC ) ;
    END COMPONENT ;
BEGIN
    Stage3: muxdff PORT MAP ( w, R(3), L, Clock, Q(3) ) ;
    Stage2: muxdff PORT MAP ( Q(3), R(2), L, Clock, Q(2) ) ;
    Stage1: muxdff PORT MAP ( Q(2), R(1), L, Clock, Q(1) ) ;
    Stage0: muxdff PORT MAP ( Q(1), R(0), L, Clock, Q(0) ) ;
END Structure ;
```

## Alternativa para o shift register

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY shift4 IS
    PORT (    R          : IN          STD_LOGIC_VECTOR(3 DOWNT0 0) ;
            Clock       : IN          STD_LOGIC ;
            L, w        : IN          STD_LOGIC ;
            Q           : BUFFER      STD_LOGIC_VECTOR(3 DOWNT0 0) ) ;
END shift4 ;

ARCHITECTURE Behavior OF shift4 IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF L = '1' THEN
            Q <= R ;
        ELSE
            Q(0) <= Q(1) ;
            Q(1) <= Q(2);
            Q(2) <= Q(3) ;
            Q(3) <= w ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

## Contador up-counter quatro-bits

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
ENTITY upcount IS
    PORT (    Clock, Resetn, E    : IN    STD_LOGIC ;
            Q                        : OUT  STD_LOGIC_VECTOR (3 DOWNT0 0)) ;
END upcount ;

ARCHITECTURE Behavior OF upcount IS
    SIGNAL Count : STD_LOGIC_VECTOR (3 DOWNT0 0) ;
BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN
            Count <= "0000" ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF E = '1' THEN
                Count <= Count + 1 ;
            ELSE
                Count <= Count ;
            END IF ;
        END IF ;
    END PROCESS ;
    Q <= Count ;
END Behavior ;
```

## Contador de 4 bits com carga paralela usando sinais INTEGER

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY upcount IS
    PORT (    R                : IN          INTEGER RANGE 0 TO 15 ;
            Clock, Resetn, L   : IN          STD_LOGIC ;
            Q                  : BUFFER      INTEGER RANGE 0 TO 15 );
END upcount ;


ARCHITECTURE Behavior OF upcount IS
BEGIN
    PROCESS ( Clock, Resetn )
    BEGIN
        IF Resetn = '0' THEN
            Q <= 0 ;
        ELSIF (Clock'EVENT AND Clock = '1') THEN
            IF L = '1' THEN
                Q <= R ;
            ELSE
                Q <= Q + 1 ;
            END IF;
        END IF;
    END PROCESS;
END Behavior;
```

## Contador down-counter


```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
ENTITY downcnt IS
    GENERIC ( modulus : INTEGER := 8 ) ;
    PORT (   Clock, L, E   : IN   STD_LOGIC ;
            Q               : OUT  INTEGER RANGE 0 TO modulus-1 ) ;
END downcnt ;

ARCHITECTURE Behavior OF downcnt IS
    SIGNAL Count : INTEGER RANGE 0 TO modulus-1 ;
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL (Clock'EVENT AND Clock = '1') ;
        IF E = '1' THEN
            IF L = '1' THEN
                Count <= modulus-1 ;
            ELSE
                Count <= Count-1 ;
            END IF ;
        END IF ;
    END PROCESS;
    Q <= Count ;
END Behavior ;
```


## Sistema digital com $k$ registradores

 

 
## Conexão dos registradores ao barramento



 
## Circuito de controle com um shift-register




# Circuito de controle modificado

 

# Cicuito de controle com FF sem preset

 
 
## Usando multiplexadores para implementação de um barramento



## Código para registrador de $n$ -bits com enable

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY regn IS
    GENERIC ( N : INTEGER := 8 ) ;
    PORT (   R           : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
            Rin, Clock   : IN      STD_LOGIC ;
            Q            : OUT     STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END regn ;

ARCHITECTURE Behavior OF regn IS
BEGIN
    PROCESS
    BEGIN
        WAIT UNTIL Clock'EVENT AND Clock = '1' ;
        IF Rin = '1' THEN
            Q <= R ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

## Código para buffer tri-sate $n$ -bits

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY trin IS
    GENERIC ( N : INTEGER := 8 ) ;
    PORT ( X   : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
           E   : IN      STD_LOGIC ;
           F   : OUT     STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
END trin ;

ARCHITECTURE Behavior OF trin IS
BEGIN
    F <= (OTHERS => 'Z') WHEN E = '0' ELSE X ;
END Behavior ;
```

## Código para controlador com for the shift-register

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY shiftr IS -- left-to-right shift register with async reset
    GENERIC ( K : INTEGER := 4 ) ;
    PORT (   Resetn, Clock, w      : IN          STD_LOGIC ;
            Q                      : BUFFER     STD_LOGIC_VECTOR(1 TO K) ) ;
END shiftr ;

ARCHITECTURE Behavior OF shiftr IS
BEGIN
    PROCESS ( Resetn, Clock )
    BEGIN
        IF Resetn = '0' THEN
            Q <= (OTHERS => '0') ;
        ELSIF Clock'EVENT AND Clock = '1' THEN
            Genbits: FOR i IN K DOWNTO 2 LOOP
                Q(i) <= Q(i-1) ;
            END LOOP ;
            Q(1) <= w ;
        END IF ;
    END PROCESS ;
END Behavior ;
```

## Declaração de package e component

```
LIBRARY ieee ;
```

```
USE ieee.std_logic_1164.all ;
```

```
PACKAGE components IS
```

```
    COMPONENT regn -- register
```

```
        GENERIC ( N : INTEGER := 8 ) ;
```

```
        PORT (    R          : IN      STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
```

```
                Rin, Clock   : IN      STD_LOGIC ;
```

```
                Q            : OUT     STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
```

```
    END COMPONENT ;
```

```
    COMPONENT shiftr -- left-to-right shift register with async reset
```

```
        GENERIC ( K : INTEGER := 4 ) ;
```

```
        PORT (    Resetn, Clock, w      : IN      STD_LOGIC ;
```

```
                Q                      : BUFFER  STD_LOGIC_VECTOR(1 TO K) ) ;
```

```
    END component ;
```

```
    COMPONENT trin -- tri-state buffers
```

```
        GENERIC ( N : INTEGER := 8 ) ;
```

```
        PORT (    X : IN  STD_LOGIC_VECTOR(N-1 DOWNT0 0) ;
```

```
                E   : IN  STD_LOGIC ;
```

```
                F   : OUT STD_LOGIC_VECTOR(N-1 DOWNT0 0) ) ;
```

```
    END COMPONENT ;
```

```
END components ;
```

## Sistema digital com bus

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.components.all ;

ENTITY swap IS
    PORT ( Data          : IN  STD_LOGIC_VECTOR(7
DOWNTO 0) ;
          Resetn, w      : IN  STD_LOGIC ;
          Clock, Extern  : IN  STD_LOGIC ;
          RinExt         : IN  STD_LOGIC_VECTOR(1 TO 3) ;
          BusWires : INOUT STD_LOGIC_VECTOR(7
DOWNTO 0) ) ;
END swap ;
```

## Sistema digital com bus - continuação

ARCHITECTURE Behavior OF swap IS

SIGNAL Rin, Rout, Q : STD\_LOGIC\_VECTOR(1 TO 3) ;

SIGNAL R1, R2, R3 : STD\_LOGIC\_VECTOR(7 DOWNT0 0) ;

BEGIN

control: shiftr GENERIC MAP ( K => 3 )

PORT MAP ( Resetn, Clock, w, Q ) ;

Rin(1) <= RinExt(1) OR Q(3) ;

Rin(2) <= RinExt(2) OR Q(2) ;

Rin(3) <= RinExt(3) OR Q(1) ;

Rout(1) <= Q(2) ; Rout(2) <= Q(1) ; Rout(3) <= Q(3) ;

tri\_ext: trin PORT MAP ( Data, Extern, BusWires ) ;

reg1: regn PORT MAP ( BusWires, Rin(1), Clock, R1 ) ;

reg2: regn PORT MAP ( BusWires, Rin(2), Clock, R2 ) ;

reg3: regn PORT MAP ( BusWires, Rin(3), Clock, R3 ) ;

tri1: trin PORT MAP ( R1, Rout(1), BusWires ) ;

tri2: trin PORT MAP ( R2, Rout(2), BusWires ) ;

tri3: trin PORT MAP ( R3, Rout(3), BusWires ) ;

END Behavior ;

## Usando multiplexadores para implementar um bus

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE work.components.all ;

ENTITY swapmux IS
    PORT ( Data      : IN      STD_LOGIC_VECTOR(7 DOWNTO 0) ;
          Resetn, w  : IN      STD_LOGIC ;
          Clock      : IN      STD_LOGIC ;
          RinExt     : IN      STD_LOGIC_VECTOR(1 TO 3) ;
          BusWires   : BUFFER  STD_LOGIC_VECTOR(7 DOWNTO 0) ) ;
END swapmux ;

ARCHITECTURE Behavior OF swapmux IS
    SIGNAL Rin, Q : STD_LOGIC_VECTOR(1 TO 3) ;
    SIGNAL S : STD_LOGIC_VECTOR(1 DOWNTO 0) ;
    SIGNAL R1, R2, R3 : STD_LOGIC_VECTOR(7 DOWNTO 0) ;
BEGIN
    control: shiftr GENERIC MAP ( K => 3 )
        PORT MAP ( Resetn, Clock, w, Q ) ;

    ... con't
```

## Usando multiplexadores para implementar um bus - continuação

```
Rin(1) <= RinExt(1) OR Q(3) ;
Rin(2) <= RinExt(2) OR Q(2) ;
Rin(3) <= RinExt(3) OR Q(1) ;
reg1: regn PORT MAP ( BusWires, Rin(1), Clock, R1 ) ;
reg2: regn PORT MAP ( BusWires, Rin(2), Clock, R2 ) ;
reg3: regn PORT MAP ( BusWires, Rin(3), Clock, R3 ) ;
encoder:
WITH Q SELECT
    S <= "00" WHEN "000",
        "10" WHEN "100",
        "01" WHEN "010",
        "11" WHEN OTHERS ;
muxes: --eight 4-to-1 multiplexers
WITH S SELECT
    BusWires <= Data WHEN "00",
        R1 WHEN "01",
        R2 WHEN "10",
        R3 WHEN OTHERS ;
END Behavior ;
```

## Código simplificado para descrever um barramento

(ENTITY declaration not shown)

ARCHITECTURE Behavior OF swapmux IS

SIGNAL Rin, Q : STD\_LOGIC\_VECTOR(1 TO 3) ;

SIGNAL R1, R2, R3 : STD\_LOGIC\_VECTOR(7 DOWNTO 0) ;

BEGIN

control: shiftr GENERIC MAP ( K => 3 )

PORT MAP ( Resetn, Clock, w, Q ) ;

Rin(1) <= RinExt(1) OR Q(3) ;

Rin(2) <= RinExt(2) OR Q(2) ;

Rin(3) <= RinExt(3) OR Q(1) ;

reg1: regn PORT MAP ( BusWires, Rin(1), Clock, R1 ) ;

reg2: regn PORT MAP ( BusWires, Rin(2), Clock, R2 ) ;

reg3: regn PORT MAP ( BusWires, Rin(3), Clock, R3 ) ;

muxes:


WITH Q SELECT

|                  |               |
|------------------|---------------|
| BusWires <= Data | WHEN "000",   |
| R2               | WHEN "100",   |
| R1               | WHEN "010",   |
| R3               | WHEN OTHERS ; |

END Behavior ;

Sistema digital implementa um processador simples


Data

 


### Operações executadas pelo processador

| Operation       | Function performed          |
|-----------------|-----------------------------|
| Load $Rx, Data$ | $Rx \leftarrow Data$        |
| Move $Rx, Ry$   | $Rx \leftarrow [Ry]$        |
| Add $Rx, Ry$    | $Rx \leftarrow [Rx] + [Ry]$ |
| Sub $Rx, Ry$    | $Rx \leftarrow [Rx] - [Ry]$ |

## Circuito de controle do processador

 
 
## Registrador de função e os decodificadores



Valores dos sinais de controle para cada operação/time step

|               | $T_1$                                | $T_2$                                  | $T_3$                            |
|---------------|--------------------------------------|----------------------------------------|----------------------------------|
| (Load): $I_0$ | $Extern, R_{in} = X,$<br>$Done$      |                                        |                                  |
| (Move): $I_1$ | $R_{in} = X, R_{out} = Y,$<br>$Done$ |                                        |                                  |
| (Add): $I_2$  | $R_{out} = X, A_{in}$                | $R_{out} = Y, G_{in},$<br>$AddSub = 0$ | $G_{out}, R_{in} = X,$<br>$Done$ |
| (Sub): $I_3$  | $R_{out} = X, A_{in}$                | $R_{out} = Y, G_{in},$<br>$AddSub = 1$ | $G_{out}, R_{in} = X,$<br>$Done$ |

## Código para two-bit up-counter reset assíncrono

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;
ENTITY upcount IS
    PORT ( Clear, Clock : IN          STD_LOGIC ;
          Q              : BUFFER STD_LOGIC_VECTOR(1 DOWNT0 0) ) ;
END upcount ;

ARCHITECTURE Behavior OF upcount IS
BEGIN
    upcount: PROCESS ( Clock )
    BEGIN
        IF (Clock'EVENT AND Clock = '1') THEN
            IF Clear = '1' THEN
                Q <= "00" ;
            ELSE
                Q <= Q + '1' ;
            END IF ;
        END IF;
    END PROCESS;
END Behavior ;
```

## Código para o processador

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_signed.all ;
USE work.subccts.all ;

ENTITY proc IS
    PORT (   Data      : IN      STD_LOGIC_VECTOR(7 DOWNTO 0) ;
            Reset, w    : IN      STD_LOGIC ;
            Clock       : IN      STD_LOGIC ;
            F, Rx, Ry   : IN      STD_LOGIC_VECTOR(1 DOWNTO 0) ;
            Done        : BUFFER  STD_LOGIC ;
            BusWires    : INOUT   STD_LOGIC_VECTOR(7 DOWNTO 0) ) ;
END proc ;

ARCHITECTURE Behavior OF proc IS
    SIGNAL Rin, Rout : STD_LOGIC_VECTOR(0 TO 3) ;
    SIGNAL Clear, High, AddSub : STD_LOGIC ;
    SIGNAL Extern, Ain, Gin, Gout, FRin : STD_LOGIC ;
    SIGNAL Count, Zero : STD_LOGIC_VECTOR(1 DOWNTO 0) ;
    SIGNAL T, I, X, Y : STD_LOGIC_VECTOR(0 TO 3) ;
    SIGNAL R0, R1, R2, R3 : STD_LOGIC_VECTOR(7 DOWNTO 0) ;
    SIGNAL A, Sum, G : STD_LOGIC_VECTOR(7 DOWNTO 0) ;
    SIGNAL Func, FuncReg : STD_LOGIC_VECTOR(1 TO 6) ;
    ... con't
```

## Código para o processador - continuação

BEGIN

```
Zero <= "00" ; High <= '1' ;
Clear <= Reset OR Done OR (NOT w AND T(0)) ;
counter: upcount PORT MAP (      Clear, Clock, Count ) ;
decT: dec2to4 PORT MAP ( Count, High, T );
Func <= F & Rx & Ry ;
FRin <= w AND T(0) ;
functionreg: regn GENERIC MAP ( N => 6 )
    PORT MAP ( Func, FRin, Clock, FuncReg ) ;
decI: dec2to4 PORT MAP ( FuncReg(1 TO 2), High, I ) ;
decX: dec2to4 PORT MAP ( FuncReg(3 TO 4), High, X ) ;
decY: dec2to4 PORT MAP ( FuncReg(5 TO 6), High, Y ) ;

Extern <= I(0) AND T(1) ;
Done <= ((I(0) OR I(1)) AND T(1)) OR ((I(2) OR I(3)) AND T(3)) ;
Ain <= (I(2) OR I(3)) AND T(1) ;
Gin <= (I(2) OR I(3)) AND T(2) ;
Gout <= (I(2) OR I(3)) AND T(3) ;
AddSub <= I(3) ;

... con't
```

## Código para o processador - continuação

```
RegCntl:
FOR k IN 0 TO 3 GENERATE
    Rin(k) <= ((I(0) OR I(1)) AND T(1) AND X(k)) OR
              ((I(2) OR I(3)) AND T(3) AND X(k)) ;
    Rout(k) <= (I(1) AND T(1) AND Y(k)) OR
              ((I(2) OR I(3)) AND ((T(1) AND X(k)) OR (T(2) AND Y(k)))) ;
END GENERATE RegCntl ;
tri_extern: trin PORT MAP ( Data, Extern, BusWires ) ;
reg0: regn PORT MAP ( BusWires, Rin(0), Clock, R0 ) ;
reg1: regn PORT MAP ( BusWires, Rin(1), Clock, R1 ) ;
reg2: regn PORT MAP ( BusWires, Rin(2), Clock, R2 ) ;
reg3: regn PORT MAP ( BusWires, Rin(3), Clock, R3 ) ;
tri0: trin PORT MAP ( R0, Rout(0), BusWires ) ;
tri1: trin PORT MAP ( R1, Rout(1), BusWires ) ;
tri2: trin PORT MAP ( R2, Rout(2), BusWires ) ;
tri3: trin PORT MAP ( R3, Rout(3), BusWires ) ;
regA: regn PORT MAP ( BusWires, Ain, Clock, A ) ;
alu:
WITH AddSub SELECT
    Sum <=  A + BusWires WHEN '0',
            A - BusWires WHEN OTHERS ;
regG: regn PORT MAP ( Sum, Gin, Clock, G ) ;
triG: trin PORT MAP ( G, Gout, BusWires ) ;
END Behavior ;
```

## Alternativa para o código do processador

... (ENTITY declaration not shown)

ARCHITECTURE Behavior OF proc IS

SIGNAL X, Y, Rin, Rout : STD\_LOGIC\_VECTOR(0 TO 3) ;

SIGNAL Clear, High, AddSub : STD\_LOGIC ;

SIGNAL Extern, Ain, Gin, Gout, FRin : STD\_LOGIC ;

SIGNAL Count, Zero, T, I : STD\_LOGIC\_VECTOR(1 DOWNT0 0) ;

SIGNAL R0, R1, R2, R3 : STD\_LOGIC\_VECTOR(7 DOWNT0 0) ;

SIGNAL A, Sum, G : STD\_LOGIC\_VECTOR(7 DOWNT0 0) ;

SIGNAL Func, FuncReg, Sel : STD\_LOGIC\_VECTOR(1 TO 6) ;

BEGIN

Zero <= "00" ; High <= '1' ;

Clear <= Reset OR Done OR (NOT w AND NOT T(1) AND NOT T(0)) ;

counter: upcount PORT MAP ( Clear, Clock, Count ) ;

T <= Count ;

Func <= F & Rx & Ry ;

FRin <= w AND NOT T(1) AND NOT T(0) ;

functionreg: regn GENERIC MAP ( N => 6 )

PORT MAP ( Func, FRin, Clock, FuncReg ) ;

I <= FuncReg(1 TO 2) ;

decX: dec2to4 PORT MAP ( FuncReg(3 TO 4), High, X ) ;

decY: dec2to4 PORT MAP ( FuncReg(5 TO 6), High, Y ) ;

controlsignals: PROCESS ( T, I, X, Y )

BEGIN

... con't

## Alternativa para o código do processador - continuação


```
Extern <= '0' ; Done <= '0' ; Ain <= '0' ; Gin <= '0' ;
Gout <= '0' ; AddSub <= '0' ; Rin <= "0000" ; Rout <= "0000" ;
CASE T IS
    WHEN "00" => -- no signals asserted in time step T0
    WHEN "01" => -- define signals asserted in time step T1
        CASE I IS
            WHEN "00" => -- Load
                Extern <= '1' ; Rin <= X ; Done <= '1' ;
            WHEN "01" => -- Move
                Rout <= Y ; Rin <= X ; Done <= '1' ;
            WHEN OTHERS => -- Add, Sub
                Rout <= X ; Ain <= '1' ;
        END CASE ;

    WHEN "10" => -- define signals asserted in time step T2
        CASE I IS
            WHEN "10" => -- Add
                Rout <= Y ; Gin <= '1' ;
            WHEN "11" => -- Sub
                Rout <= Y ; AddSub <= '1' ; Gin <= '1' ;
            WHEN OTHERS => -- Load, Move
        END CASE ;
    WHEN OTHERS => -- define signals asserted in time step T3
        CASE I IS
```


## Alternativa para o código do processador - continuação

```
        WHEN "00" => -- Load
        WHEN "01" => -- Move
        WHEN OTHERS => -- Add, Sub
            Gout <= '1' ; Rin <= X ; Done <= '1' ;
    END CASE ;
END CASE ;
END PROCESS ;
reg0: regn PORT MAP ( BusWires, Rin(0), Clock, R0 ) ;
reg1: regn PORT MAP ( BusWires, Rin(1), Clock, R1 ) ;
reg2: regn PORT MAP ( BusWires, Rin(2), Clock, R2 ) ;
reg3: regn PORT MAP ( BusWires, Rin(3), Clock, R3 ) ;
regA: regn PORT MAP ( BusWires, Ain, Clock, A ) ;
alu: WITH AddSub SELECT
    Sum <=    A + BusWires WHEN '0',
             A - BusWires WHEN OTHERS ;
regG: regn PORT MAP ( Sum, Gin, Clock, G ) ;
Sel <= Rout & Gout & Extern ;
WITH Sel SELECT
    BusWires <=    R0  WHEN "100000",
                  R1  WHEN "010000",
                  R2  WHEN "001000",
                  R3  WHEN "000100",
                  G   WHEN "000010",
                  Data WHEN OTHERS ;
END Behavior ;
```

## Um circuito reaction-timer

 


(a) Clock divider

 

(b) LED circuit

## Um circuito reaction-timer

 

(c) Push-button switch, LED, and 7-segment displays

## Código para contador BCD de dois dígitos

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;
USE ieee.std_logic_unsigned.all ;

ENTITY BCDcount IS
    PORT ( Clock      : IN      STD_LOGIC ;
          Clear, E     : IN      STD_LOGIC ;
          BCD1, BCD0 : BUFFER  STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
END BCDcount ;

ARCHITECTURE Behavior OF BCDcount IS
BEGIN
    PROCESS ( Clock )
    BEGIN
        IF Clock'EVENT AND Clock = '1' THEN
            IF Clear = '1' THEN
                BCD1 <= "0000" ; BCD0 <= "0000" ;
            ... con't
```

## Código para contador BCD de dois dígitos

```
ELSIF E = '1' THEN
    IF BCD0 = "1001" THEN
        BCD0 <= "0000" ;
        IF BCD1 = "1001" THEN
            BCD1 <= "0000";
        ELSE
            BCD1 <= BCD1 + '1' ;
        END IF ;
    ELSE
        BCD0 <= BCD0 + '1' ;
    END IF ;
END IF ;
END IF;
END PROCESS;
END Behavior ;
```

## Código para o reaction timer

```
LIBRARY ieee ;
USE ieee.std_logic_1164.all ;

ENTITY reaction IS
    PORT ( c9, Reset      : IN          STD_LOGIC ;
           w, Pushn       : IN          STD_LOGIC ;
           LEDn           : OUT         STD_LOGIC ;
           Digit1, Digit0 : BUFFER     STD_LOGIC_VECTOR(1 TO 7) ) ;
END reaction ;

ARCHITECTURE Behavior OF reaction IS
    COMPONENT BCDcount
        PORT ( Clock      : IN          STD_LOGIC ;
              Clear, E     : IN          STD_LOGIC ;
              BCD1, BCD0   : BUFFER     STD_LOGIC_VECTOR(3 DOWNTO 0) ) ;
    END COMPONENT ;
    COMPONENT seg7
        PORT ( bcd      : IN          STD_LOGIC_VECTOR(3 DOWNTO 0) ;
              leds      : OUT         STD_LOGIC_VECTOR(1 TO 7) ) ;
    END COMPONENT ;
    SIGNAL LED : STD_LOGIC ;
    SIGNAL BCD1, BCD0 : STD_LOGIC_VECTOR(3 DOWNTO 0) ;
```

... con't

## Código para o reaction timer (continuação)

```
BEGIN
  flipflop: PROCESS
  BEGIN
    WAIT UNTIL c9'EVENT AND c9 = '1' ;
    IF Pushn = '0' THEN
      LED <= '0' ;
    ELSIF w = '1' THEN
      LED <= '1' ;
    END IF ;
  END PROCESS ;

  LEDn <= NOT LED ;
  counter: BCDcount PORT MAP ( c9, Reset, LED, BCD1, BCD0 ) ;
  seg1 : seg7 PORT MAP ( BCD1, Digit1 ) ;
  seg0 : seg7 PORT MAP ( BCD0, Digit0 ) ;
END Behavior ;
```