 





(a) Two states of a switch




(b) Symbol for a switch

Figure 2.1 A binary switch

 


(a) Simple connection to a battery

 


(b) Using a ground connection as the return path

Figure 2.2 A light controlled by a switch

 

 (a) The logical AND function (series connection)



(b) The logical OR function (parallel connection)

Figure 2.3 Two basic functions

 


Figure 2.4 A series-parallel connection

 


Figure 2.5 An inverting circuit

$x_1$	$x_2$	$x_1 \cdot x_2$	$x_1 + x_2$
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	1


AND

OR


Figure 2.6 A truth table for AND and OR

$x_1$	$x_2$	$x_3$	$x_1 \cdot x_2 \cdot x_3$	$x_1 + x_2 + x_3$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	0	1
1	0	0	0	1
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1


Figure 2.7 Three-input AND and OR

 

(a) AND gates

 

(b) OR gates

 

(c) NOT gate

Figure 2.8 The basic gates




 


Figure 2.9 An OR-AND function

 


(a) Network that implements  $f = \bar{x}_1 + x_1 \cdot x_2$


$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

(b) Truth table for  $f$

Figure 2.10 a Logic network

 

(c) Timing diagram

 

(d) Network that implements  $g = \bar{x}_1 + x_2$

Figure 2.10 b Logic network

$x$	$y$	$x \cdot y$	$\overline{x \cdot y}$	$\bar{x}$	$\bar{y}$	$\bar{x} + \bar{y}$
0	0	0	1	1	1	1
0	1	0	1	1	0	1
1	0	0	1	0	1	1
1	1	1	0	0	0	0

⏟
⏟  
 LHS                      RHS

Figure 2.11 Proof of DeMorgan's theorem

Please see “**portrait orientation**” PowerPoint file for Chapter 2

Figure 2.12 The Venn diagram representation

Please see “**portrait orientation**” PowerPoint file for Chapter 2

Figure 2.13 Verification of the distributive property


Please see “**portrait orientation**” PowerPoint file for Chapter 2

Figure 2.14 Verification example


$x_1$	$x_2$	$f(x_1, x_2)$
0	0	1
0	1	1
1	0	0
1	1	1

Figure 2.15 A function to be synthesized



 

(a) Canonical sum-of-products

 

(b) Minimal-cost realization


Figure 2.16 Two implementations of a function

Row number	$x_1$	$x_2$	$x_3$	Minterm	Maxterm
0	0	0	0	$m_0 = \bar{x}_1 \bar{x}_2 \bar{x}_3$	$M_0 = x_1 + x_2 + x_3$
1	0	0	1	$m_1 = \bar{x}_1 \bar{x}_2 x_3$	$M_1 = x_1 + x_2 + \bar{x}_3$
2	0	1	0	$m_2 = \bar{x}_1 x_2 \bar{x}_3$	$M_2 = x_1 + \bar{x}_2 + x_3$
3	0	1	1	$m_3 = \bar{x}_1 x_2 x_3$	$M_3 = x_1 + \bar{x}_2 + \bar{x}_3$
4	1	0	0	$m_4 = x_1 \bar{x}_2 \bar{x}_3$	$M_4 = \bar{x}_1 + x_2 + x_3$
5	1	0	1	$m_5 = x_1 \bar{x}_2 x_3$	$M_5 = \bar{x}_1 + x_2 + \bar{x}_3$
6	1	1	0	$m_6 = x_1 x_2 \bar{x}_3$	$M_6 = \bar{x}_1 + \bar{x}_2 + x_3$
7	1	1	1	$m_7 = x_1 x_2 x_3$	$M_7 = \bar{x}_1 + \bar{x}_2 + \bar{x}_3$


Figure 2.17 Three-variable Minterms and Maxterms

Row number	$x_1$	$x_2$	$x_3$	$f(x_1, x_2, x_3)$
0	0	0	0	0
1	0	0	1	1
2	0	1	0	0
3	0	1	1	0
4	1	0	0	1
5	1	0	1	1
6	1	1	0	1
7	1	1	1	0

Figure 2.18 A three-variable function

 

 (a) A minimal sum-of-products realization




(b) A minimal product-of-sums realization

Figure 2.19 Two realizations of a function


$x_1$	$x_2$	$x_3$	$f$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

Figure 2.20 Truth table for a three-way light controller

 

(a) Sum-of-products realization

Figure 2.21 SOP implementation of the three-way light controller

 


(b) Product-of-sums realization


Figure 2.21 POS implementation of the three-way light controller

$s$	$x_1$	$x_2$	$f(s, x_1, x_2)$
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

(a) Truth table

 

(b) Circuit

 

(c) Graphical symbol

$s$	$f(s, x_1, x_2)$
0	$x_1$
1	$x_2$

(d) More compact truth-table representation

Figure 2.22 Multiplexer



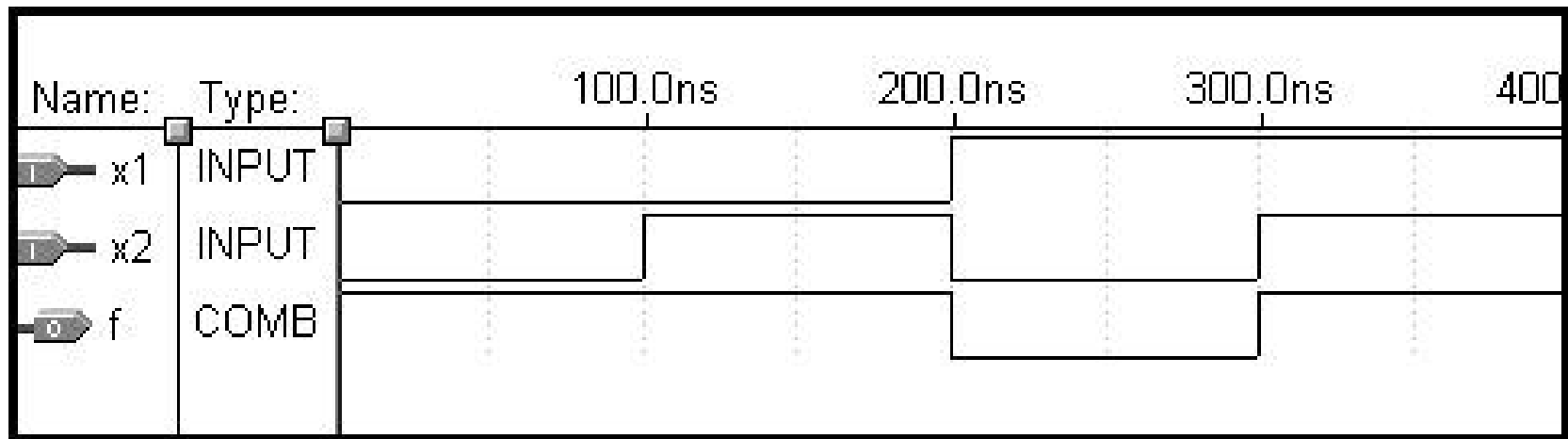


Figure 2.23 Screen capture of the Waveform Editor


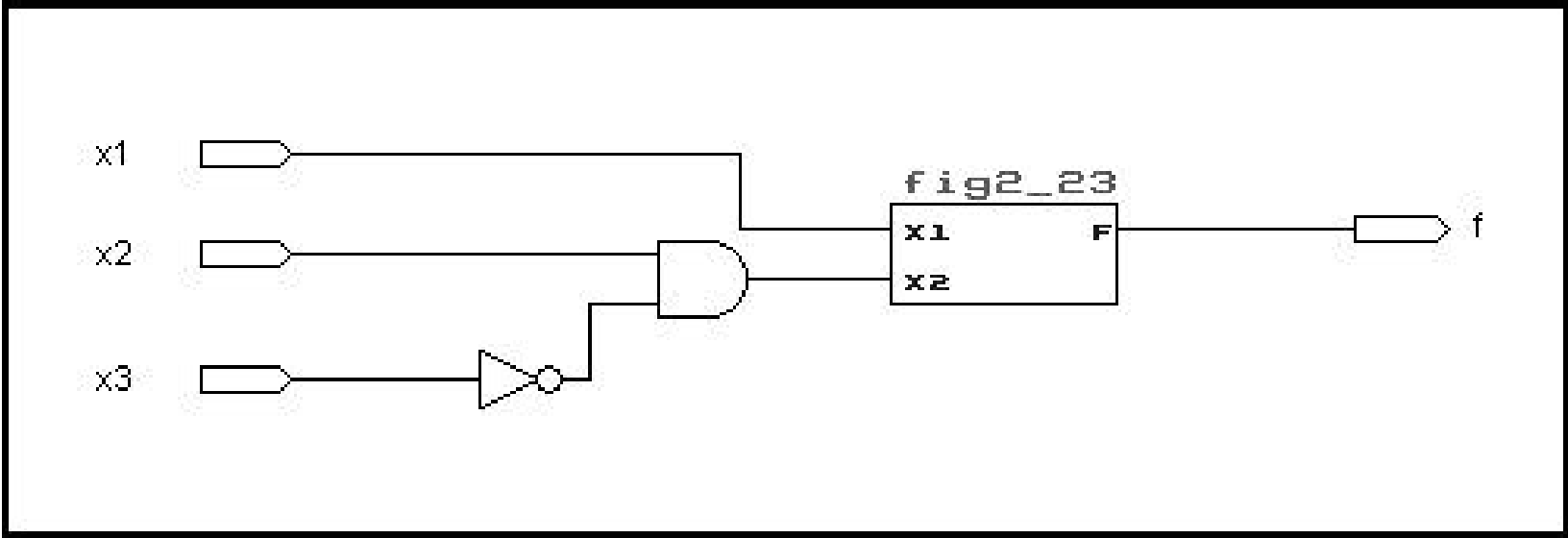


Figure 2.24 Screen capture of the Graphic Editor

Please see “**portrait orientation**” PowerPoint file for Chapter 2

Figure 2.25 The first stages of a CAD system

 

```

ENTITY example1 IS
    PORT ( x1, x2, x3  : IN    BIT ;
          f           : OUT  BIT ) ;
END example1 ;

ARCHITECTURE LogicFunc OF example1 IS
BEGIN
    f <= (x1 AND x2) OR (NOT x2 AND x3) ;
END LogicFunc ;

```

Figure 2.26 A simple logic function and corresponding VHDL code

```

ENTITY example2 IS
    PORT ( x1, x2, x3, x4 : IN    BIT ;
          f, g           : OUT  BIT ) ;
END example2 ;

ARCHITECTURE LogicFunc OF example2 IS
BEGIN
    f <= (x1 AND x3) OR (NOT x3 AND x2) ;
    g <= (NOT x3 OR x1) AND (NOT x3 OR x4) ;
END LogicFunc ;

```

Figure 2.30 VHDL code for a four-input function



 


Figure 2. 31 Logic circuit for four-input function

 

(a)

 

(b)

Figure P2.1 Two attempts to draw a four-variable Venn diagram

 


Figure P2.2 A four-variable Venn diagram



 


Figure P2.3 A timing diagram representing a logic function

 


Figure P2.4 A timing diagram representing a logic function