 



Figure 3.1 Logic values as voltage levels



(a) A simple switch controlled by the input  $x$



(b) NMOS transistor

 


(c) Simplified symbol for an NMOS transistor


Figure 3.2 NMOS transistor as a switch



 (a) A switch with the opposite behavior of Figure 3.2 a



(b) PMOS transistor

 

(c) Simplified symbol for an PMOS transistor

Figure 3.3 PMOS transistor as a switch



 
 



Figure 3.4 NMOS and PMOS transistors in logic circuits

 

(a) Circuit diagram

 


(b) Simplified circuit diagram

 

(c) Graphical symbols


Figure 3.5 A NOT gate built using NMOS technology

 

(a) Circuit


$x_1$	$x_2$	$f$
0	0	1
0	1	1
1	0	1
1	1	0

(b) Truth table

 

(c) Graphical symbols


Figure 3.6 NMOS realization of a NAND gate

 

(a) Circuit


$x_1$	$x_2$	$f$
0	0	1
0	1	0
1	0	0
1	1	0

(b) Truth table

 

(c) Graphical symbols


Figure 3.7 NMOS realization of a NOR gate

 

(a) Circuit

$x_1$	$x_2$	$f$
0	0	0
0	1	0
1	0	0
1	1	1

(b) Truth table

 

(c) Graphical symbols

Figure 3.8 NMOS realization of an AND gate

 
 


Figure 3.9 NMOS realization of an OR gate

 


Figure 3.10 Structure of an NMOS circuit


 


Figure 3.11 Structure of a CMOS circuit

 


(a) Circuit

$x$	$T_1$	$T_2$	$f$
0	on	off	1
1	off	on	0

(b) Truth table and transistor states

Figure 3.12 CMOS realization of a NOT gate

 


(a) Circuit

$x_1$	$x_2$	$T_1$	$T_2$	$T_3$	$T_4$	$f$
0	0	on	on	off	off	1
0	1	on	off	off	on	1
1	0	off	on	on	off	1
1	1	off	off	on	on	0

(b) Truth table and transistor states

Figure 3.13 CMOS realization of a NAND gate

 

(a) Circuit

$x_1$	$x_2$	$T_1$	$T_2$	$T_3$	$T_4$	$f$
0	0	on	on	off	off	1
0	1	on	off	off	on	0
1	0	off	on	on	off	0
1	1	off	off	on	on	0

(b) Truth table and transistor states

Figure 3.14 CMOS realization of a NOR gate

 


Figure 3.15 CMOS realization of an AND gate

 


Figure 3.16 A CMOS complex gate

 


Figure 3.17 A CMOS complex gate


 


Figure 3.18 Voltage levels in a CMOS circuit

$V_{x_1}$	$V_{x_2}$	$V_f$
L	L	H
L	H	H
H	L	H
H	H	L


(a) Voltage levels

$x_1$	$x_2$	$f$
0	0	1
0	1	1
1	0	1
1	1	0

 

(b) Positive logic truth table and gate symbol

$x_1$	$x_2$	$f$
1	1	0
1	0	0
0	1	0
0	0	1

 


(c) Negative logic truth table and gate symbol

Figure 3.19 Interpretation of voltage levels

$V_{x_1}$	$V_{x_2}$	$V_f$
L	L	L
L	H	L
H	L	L
H	H	H

(a) Voltage levels

$x_1$	$x_2$	$f$
0	0	0
0	1	0
1	0	0
1	1	1

 


(b) Positive logic

$x_1$	$x_2$	$f$
1	1	1
1	0	1
0	1	1
0	0	0




(c) Negative logic

Figure 3.20 Interpretation of voltage levels

 

(a) Dual-inline package

 

(b) Structure of 7404 chip

Figure 3.21 A 7400-series chip

 


Figure 3.22 Implementation of  $f = x_1\bar{x}_2 + x_2x_3$

 


Figure 3.23 The 74244 buffer chip

 


Figure 3.24 Programmable logic device as a black box

 


Figure 3.25 General structure of a PLA

 


Figure 3.26 Gate-level diagram of a PLA

 


Figure 3.27 Customary schematic of a PLA

 


Figure 3.28 An example of a PLA

 


Figure 3.29 Output circuitry



Figure 3.30 A PLD programming unit

 


Figure 3.31 A PLCC package with socket

 


Figure 3.32 Structure of a CPLD



 


Figure 3.33 A section of a CPLD

 

 (a) CPLD in a Quad Flat Pack (QFP) package



(b) JTAG programming

Figure 3.34 CPLD packaging and programming


 



Figure 3.35 Structure of an FPGA

 

(a) Circuit for a two-input LUT

$x_1$	$x_2$	$f_1$
0	0	1
0	1	0
1	0	0
1	1	1

 (b)  $f_1 = \bar{x}_1 \bar{x}_2 + x_1 x_2$



(c) Storage cell contents in the LUT

Figure 3.36 A two-input lookup table

 


Figure 3.37 A three-input LUT

 


Figure 3.38 Inclusion of a flip-flop with a LUT

 


Figure 3.39 A section of a programmed FPGA

 


Figure 3.40 A section of two rows in a standard-cell chip

 


Figure 3.41 A sea-of-gates gate array



 


Figure 3.42 An example of a logic function in a gate array

 

(a) When  $V_{GS} = 0 \text{ V}$ , the transistor is off

Figure 3.43 a NMOS transistor when turned off

 

(b) When  $V_{GS}= 5 \text{ V}$ , the transistor is on

Figure 3.43 b NMOS transistor when turned on



 


Figure 3.44 Current-voltage relationship in the NMOS transistor

 

(a) NMOS NOT gate

 

(b)  $V_x = 5 \text{ V}$

Figure 3.45 Voltage levels in the NMOS inverter



 


Figure 3.46 Voltage transfer characteristics for the CMOS inverter

 

(a) A NOT gate driving another NOT gate

 

(b) The capacitive load at node A

Figure 3.47 Parasitic capacitance in integrated circuits



 


Figure 3.48 Voltage waveforms for logic gates

 


(a) Small transistor

 


(b) Larger transistor

Figure 3.49 Transistor sizes

 

 (a) Current flow when input  $V_x$   
changes from 0 V to 5 V



(b) Current flow when input  $V_x$   
changes from 5 V to 0 V

Figure 3.50 Dynamic current flow in CMOS circuits


 


Figure 3.51 Poor use of NMOS and PMOS transistors

 

(a) An AND gate circuit

Logic value		Voltage	Logic value
$x_1$	$x_2$	$V_f$	$f$
0	0	1.5 V	0
0	1	1.5 V	0
1	0	1.5 V	0
1	1	3.5 V	1

(b) Truth table and voltage levels

Figure 3.52 Poor implementation of a CMOS AND gate

 


Figure 3.53 High fan-in NMOS NAND gate



 


Figure 3.54 High fan-in NMOS NOR gate

 


To inputs of  
 $n$  other inverters

 


(a) Inverter that drives  $n$  other inverters

 (b) Equivalent circuit for timing purposes




(c) Propagation times for different values of  $n$

Figure 3.55 The effect of fan-out on propagation delay

 


(a) Implementation of a buffer

 


(b) Graphical symbol

Figure 3.56 A noninverting buffer

 


(a) A tri-state buffer

 

(b) Equivalent circuit


e	x	f
0	0	Z
0	1	Z
1	0	0
1	1	1

(c) Truth table

 


(d) Implementation


Figure 3.57 Tri-state buffer

 


(a)

 

(b)

 

(c)

 

(d)

Figure 3.58 Four types of tri-state buffers


 



Figure 3.59 An application of tri-state buffers

 


(a) Circuit

$\bar{s}$	$f$
0	$Z$
1	$x$

(b) Truth table

 

(c) Equivalent circuit

 


(d) Graphical symbol


Figure 3.60 A transmission gate

$x_1$	$x_2$	$f = x_1 \oplus x_2$
0	0	0
0	1	1
1	0	1
1	1	0

(a) Truth table

 


(b) Graphical symbol

 

(c) Sum-of-products implementation

Figure 3.61 a Exclusive-OR gate

 

(d) CMOS implementation

Figure 3.61 b CMOS Exclusive-OR gate

 


Figure 3.62 A 2-to-1 multiplexer built using transmission gates

 


Figure 3.63 An example of a NOR-NOR PLA

Please see “**portrait orientation**” PowerPoint file for Chapter 3

Figure 3.64 A programmable NOR plane

 


Figure 3.65 A programmable version of a NOR-NOR PLA

 


Figure 3.66 A NOR-NOR PLA used for sum-of-products

 


Figure 3.67 PAL programmed to implement two functions

 


Figure 3.68 Pass-transistor switches in FPGAs

 


Figure 3.69 Restoring a high voltage level

 


Figure P3.1 A sum-of-products CMOS circuit

 


Figure P3.2 A CMOS circuit built with multiplexers

 


Figure P3.3 Circuit for problem 3.3

 


Figure P3.4 A three-input CMOS circuit

 


Figure P3.5 A four-input CMOS circuit

 


Figure P3.6 The pull-down network in a CMOS circuit

 


Figure P3.7 The pull-up network in a CMOS circuit

 


Figure P3.8 The pseudo-NMOS inverter

 


Figure P3.9 A gate-array logic cell

 


Figure P3.10 Circuit for problem 3.54

 


Figure P3.11 Circuit for problem 3.55