
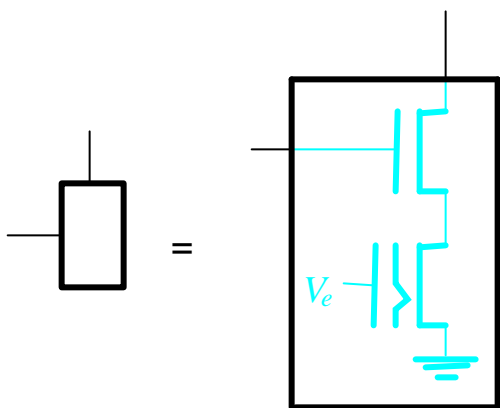


(a) Programmable NOR-plane

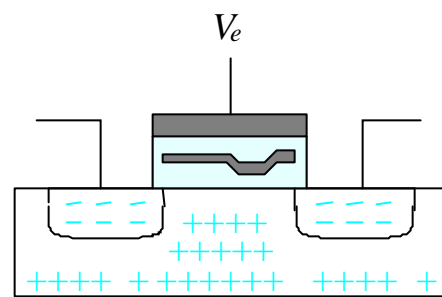

(b) A programmable switch



(c) EEPROM transistor

Figure 3.64 A programmable NOR plane